 


## Binary Logic and Boolean algebra

**Boolean algebra:** Devised for dealing mathematically with philosophical propositions which have **ONLY TWO** possible values: **TRUE** or **FALSE**, **Light ON** or **OFF**.



**SW1 Open** >> Lamp is **OFF**

**SW1 Closed** >> Lamp is **ON**

Two states:

<b>SW1</b>	<b>Lamp</b>
OPEN	OFF
CLOSED	ON

“Truth Table”

## **Electronic Systems:**

Analog >> **Continuous System**

Digital >> **Discrete System**

In Boolean algebra the TWO possible conditions can be represented by the DIGITS “0” and “1”.

Binary Digits – Bits.

Light ON = “1” = +5V = HIGH

Light OFF = “0” = 0V = LOW

If we define:

Open = “0”, CLOSED = “1”


Then:

<b>SW1</b>	<b>Lamp</b>
0	0
1	1

Boolean algebra deals with the rules which govern various operations between the binary variables.

**“AND” operation:** Describes events which can occur **IF and only IF** 2 or more other events are TRUE.

Consider:

 

The truth table is:

A	B	L
OPEN	OPEN	OFF
OPEN	CLOSED	OFF
CLOSED	OPEN	OFF
CLOSED	CLOSED	ON

A	B	L
0	0	0
0	1	0
1	0	0
1	1	1

Lamp will light **ONLY** when the switches A and B are **CLOSED**, i.e. A and B both “1”

**NOTATION:**  $C = A.B$

$C = AB$

**Boolean Equation**


SYMBOL: **AND** gate:



THE "AND" GATE

**“OR” Operation:** Describes events which can occur **IF at LEAST ONE** of the other events are TRUE.

Consider:

 

Switches in parallel, lamp will light when A OR B are closed, i.e. A or B = “1” or Both “1”

A	B	L
OPEN	OPEN	OFF
OPEN	CLOSED	ON
CLOSED	OPEN	ON
CLOSED	CLOSED	ON

A	B	L
0	0	0
0	1	1
1	0	1
1	1	1

**NOTATION:**  $C = A + B$


**SYMBOL:** **OR** gate:



THE "OR" GATE

**“NOT” operation:** Changes a statement from TRUE to FALSE and vice-versa, i.e. inversion

Consider:

 

The Truth table is:


<b>A</b>	<b>L</b>
OPEN	ON
CLOSED	OFF

<b>A</b>	<b>L</b>
0	1
1	0

When A is **CLOSED** virtually NO CURRENT flows through L, so it is effectively **OFF**.

**NOTATION:**  $C = \bar{A}$

**SYMBOL:** **NOT** gate

 

# BASIC LAWS OF BOOLEAN ALGEBRA

## 1. COMUTATIVE LAW:

$$A + B = B + A$$

$$A \cdot B = B \cdot A$$

## 2. ASSOCIATIVE LAW:


$$A + (B + C) = (A + B) + C$$

$$A(BC) = (AB)C$$
 
## 3. DISTRIBUTIVE LAW:

$$A(B + C) = AB + AC$$

THESE LAWS CAN BE **EXTENDED** TO INCLUDE ANY NUMBER OF VARIABLES.



## BASIC RULES OF BOOLEAN ALGEBRA

1.  $A + 0 = A$

2.  $A + 1 = 1$

3.  $A \cdot 0 = 0$

4.  $A \cdot 1 = A$

5.  $A + \bar{A} = 1$

6.  $A \cdot \bar{A} = 0$

7.  $\overline{\bar{A}} = A$

8.  $A + AB = A$

9.  $A + \bar{A}B = A + B$

10.  $(A+B)(A+C) = A+BC$



## PROOF OF RULES 10, 11, 12:

$$\begin{aligned}
 \textbf{Rule 10: } A+AB &= A(1+B) \\
 &= A \cdot 1 && \text{(Rule 2)} \\
 &= A && \text{(Rule 4)}
 \end{aligned}$$

$$\begin{aligned}
 \textbf{Rule 11: } A + \overline{A}B &= \\
 &= (A + AB) + \overline{A}B && \text{(Rule 10)} \\
 &= (AA + AB) + \overline{A}B && \text{(Rule 7)} \\
 &= AA + AB + A\overline{A} + \overline{A}B && \text{(Rule 8)} \\
 &\quad \text{i.e. adding } A\overline{A} = 0 \\
 &= (A+\overline{A})(A + B) && \text{(Factoring)} \\
 &= 1 \cdot (A + B) && \text{(Rule 6)} \\
 &= A + B
 \end{aligned}$$

$$\begin{aligned}
 \textbf{Rule 12: } (A + B)(A + C) &= \\
 &= AA + AC + AB + BC && \text{(Distrib.)} \\
 &= A + AC + AB + BC && \text{(Rule 7)} \\
 &= A(1+C) + AB + BC && \text{(Distrib.)} \\
 &= A \cdot 1 + AB + BC && \text{(Rule 4)} \\
 &= A + AB + BC && \text{(Rule 2)} \\
 &= A(1 + B) + BC && \text{(Distrib.)} \\
 &= A \cdot 1 + BC && \text{(Rule 2)} \\
 &= A + BC && \text{(Rule 4)}
 \end{aligned}$$

## DE MORGAN'S THEOREMS

$$1. \overline{AB} = \overline{A} + \overline{B}$$

THIS STATES THAT THE INVERSE (i.e.) OF A PRODUCT [AND] IS EQUAL TO THE SUM [OR] OF THE COMPLEMENTS

$$2. \overline{A + B} = \overline{A} . \overline{B}$$

THIS STATES THAT THE INVERSE (COMPLEMENT) OF A SUM [OR] IS EQUAL TO THE PRODUCT [AND] OF THE COMPLEMENTS

## TWO VERY IMPORTANT THEOREMS


THESE THEOREMS CAN BE EXTENDED TO COVER SEVERAL VARIABLES:

$$\overline{ABC} = \overline{A} + \overline{B} + \overline{C}$$


$$\overline{A + B + C} = \overline{A} . \overline{B} . \overline{C}$$

## PROOF OF (1): $\overline{AB} = \overline{A} + \overline{B}$

<b>A</b>	<b>B</b>	<b>AB</b>	<b><math>\overline{AB}</math></b>	<b><math>\overline{A}</math></b>	<b><math>\overline{B}</math></b>	<b><math>\overline{A} + \overline{B}</math></b>
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

 


=

 


**PROOF OF (2):  $\overline{A + B} = \bar{A} \cdot \bar{B}$**

<b>A</b>	<b>B</b>	<b>A+B</b>	<b><math>\bar{A}</math></b>	<b><math>\bar{B}</math></b>	<b><math>\overline{A+B}</math></b>	<b><math>\bar{A} \cdot \bar{B}</math></b>
0	0	0	1	1	1	1
0	1	1	1	0	0	0
1	0	1	0	1	0	0
1	1	1	0	0	0	0

 

=

 

## “EXCLUSIVE OR” OPERATION

EVENTS WHICH ARE TRUE ONLY IF AND ONLY IF ONE OF THE MOTIVATING EVENTS ARE TRUE


ABBREVIATED: **XOR**

TRUTH TABLE:

<b>A</b>	<b>B</b>	<b>A “XOR” B</b>
0	0	0
0	1	1
1	0	1
1	1	0


NOTATION:  **$F = A \oplus B$**

SYMBOL:

 

**F="1" IF A="1" OR B="1" BUT NOT  
A = B = "1"**

$$\gg F = (A + B)(\overline{AB})$$

 


### ANOTHER WAY OF EXPRESSING XOR

$$F = (A + B)(\overline{AB})$$

$$= (A + B)(\overline{A} + \overline{B}) \quad (\text{De Morgan})$$

$$= A\overline{A} + A\overline{B} + A\overline{B} + B\overline{B} \quad (\text{Distrib.})$$
 
$$= A\overline{B} + \overline{A}B \quad (\text{Rule 8})$$



## “NAND” OPERATION

DE MORGAN’S THEOREMS MEANS THAT ANY BOOLEAN OPERATION CAN BE PERFORMED BY A COMBINATION OF “AND” AND “NOT” OPERATIONS


A VERY USEFUL OPERATION IS THE “NAND” i.e. AN “AND” OPERATION FOLLOWED BY A “NOT” OPERATION

TRUTH TABLE:

<b>A</b>	<b>B</b>	<b>A “NAND” B</b>
0	0	1
0	1	1
1	0	1
1	1	0


NOTATION:  $F = \overline{A \cdot B}$

## SYMBOL NAND GATE:

 


**IMPORTANT NOTE: ANY BOOLEAN FUNCTION MAY BE IMPLEMENTED USING ONLY NAND GATES!**

### 1. “NOT” GATE (INVERTER)

 




## 2. "AND" GATE

 

## 3. "OR" GATE

 

## “NOR” OPERATION

FROM DE MORGAN’S THEOREMS, WE ALSO CAN EXPRESS ANY BOOLEAN FUNCTION IN TERMS OF “OR” AND “NOT” OPERATIONS


A “NOR” OPERATION IS A “OR” OPERATION FOLLOWED BY A “NOT” OPERATION

TRUTH TABLE:


A	B	A “NOR” B
0	0	1
0	1	0
1	0	0
1	1	0

NOTATION:  $F = \overline{A + B}$


SYMBOL: NOR GATE

 


## 1. "NOT" GATE (INVERTER)

 

## 2. "OR" GATE

 


## 3. "AND" GATE

 

 **ANY COMPLEX BOOLEAN FUNCTION CAN BE IMPLEMENTED USING ONLY NOR GATES.**


**E.G. >>  $F = \overline{\overline{(A + B)}(C + D)}$**   
 **$= \overline{(A + B) + (C + D)}$**



**IN PRACTICE “NAND” GATES ARE USED MAINLY (E.G. 7400) AS THEY ARE THE CHEAPEST.**

**EXAMPLE 1: IMPLEMENT THE “XOR” OPERATION USING “NAND” GATES.**


$$F = A \oplus B = A\bar{B} + \bar{A}B = \overline{\overline{A\bar{B}}} \cdot \overline{\overline{\bar{A}B}}$$

 

 **EXAMPLE 2: IMPLEMENT THE FOLLOWING AND-OR FUNCTION USING “NAND” GATES:**

$$F = AB + CD$$

$$F = AB + CD = \overline{\overline{AB} \cdot \overline{CD}}$$



## SUMMARY

- **BOOLEAN ALGEBRA: SYMBOLS, RULES**
- **EXPRESS THE LOGICAL FUNCTIONS AND, OR, NOT, XOR, NAND AND NOR MATHEMATICALLY**
- **BASIC LAWS OF BOOLEAN ALGEBRA AND HOW TO APPLY THEM.**
- **DE MORGAN'S THEOREMS AND HOW TO APPLY THEM.**

## **LOGIC DESIGN**

**AIM:** TO DESIGN DIGITAL SYSTEMS USING THE RULES OF BOOLEAN ALGEBRA (FLOYD 4-5/4-6).

### **DESIGNING A LOGIC SYSTEM:**

1. **DEFINE** THE PROBLEM
2. **WRITE** THE TRUTH TABLE
3. **WRITE** THE BOOLEAN (OR LOGIC) EQUATIONS
4. **SIMPLIFY** EQUATIONS TO MINIMISE THE NUMBER OF GATES
5. **DRAW** A LOGIC DIAGRAM
6. **IMPLEMENT** THE LOGIC DIAGRAM USING ELECTRONIC CIRCUITRY

NEXT, WE WILL INVESTIGATE **MINIMISATION TECHNIQUES** USING BOOLEAN ALGEBRA LAWS.

## EXAMPLE 1:

WE HAVE A CAR WITH 3 MAIN CONTROL SYSTEMS. WE WANT A WARNING LAMP TO LIGHT IF ANY OF THE FOLLOWING CONDITIONS OCCUR:

1. ALL SYSTEMS ARE DOWN
2. SYSTEMS A,B DOWN BUT C IS OK
3. SYSTEMS A,C DOWN BUT B IS OK
4. SYSTEM A DOWN BUT B,C ARE OK

### 1. DEFINE THE PROBLEM

NOTE: THERE ARE TWO POSSIBLE STATES FOR EACH SYSTEM.

ASSIGN:

SYSTEM: **DOWN** = "0",     **OK** = "1"

LIGHT:     **OFF** = "0",     **ON** = "1"



**LOGIC BLOCK DIAGRAM**



## 1. TRUTH TABLE

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0


## 3. WRITE LOGIC EQUATIONS

$$F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC$$

## 4. SIMPLYFY EQUATIONS

$$\begin{aligned}
 F &= \bar{A}(\bar{B}\bar{C} + \bar{B}C + B\bar{C} + BC) \\
 &= \bar{A}[\bar{B}(\bar{C} + C) + B(\bar{C} + C)] \\
 &= \bar{A}(\bar{B} \cdot 1 + B \cdot 1) \\
 &= \bar{A}(\bar{B} + B) \\
 &= \bar{A} \cdot 1 = \bar{A} \quad \gg \quad F = \bar{A}
 \end{aligned}$$

## 5. LOGIC DIAGRAM

 

### **EXAMPLE 2:**

4 SYSTEMS : **A, B, C AND D**

A WARNING BUZZER IS TO SOUND WHEN THE FOLLOWING CONDITIONS OCCUR.

- (a) **A AND B ARE DOWN**
- (b) **A,C AND D ARE DOWN**
- (c) **B,C AND D ARE DOWN**
- (d) **B AND D ARE DOWN**

### **1. DEFINE THE PROBLEM**

SYSTEM: **DOWN = "0", OK = "1"**

BUZZER: **OFF = "0", ON = "1"**



## 2. TRUTH TABLE:

<b>A</b>	<b>B</b>	<b>C</b>	<b>D</b>	<b>F</b>
0	0	0	0	<b>1</b> (a) (d)
0	0	0	1	<b>1</b> (a)
0	0	1	0	<b>1</b> (a) (d)
0	0	1	1	<b>1</b> (a)
0	1	0	0	<b>1</b> (b)
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	<b>1</b> (c) (d)
1	0	0	1	0
1	0	1	0	<b>1</b> (d)
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

## 3. LOGIC EQUATION:

$$\begin{aligned}
 F = & \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD \\
 & + \bar{A}B\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D}
 \end{aligned}$$

#### 4. SYMPLIFY:

$$\begin{aligned}
 F &= \bar{A}\bar{B}\bar{C}(\bar{D} + D) + \bar{A}\bar{B}C(\bar{D} + D) + \bar{A}B\bar{C}\bar{D} \\
 &\quad + A\bar{B}\bar{D}(\bar{C} + C) \\
 &= \bar{A}\bar{B}\bar{C} \cdot 1 + \bar{A}\bar{B}C \cdot 1 + A\bar{B}\bar{D} + \bar{A}B\bar{C}\bar{D} \\
 &= \bar{A}\bar{B}(\bar{C} + C) + A\bar{B}\bar{D} + \bar{A}B\bar{C}\bar{D} \\
 &= \bar{A}\bar{B} \cdot 1 + A\bar{B}\bar{D} + \bar{A}B\bar{C}\bar{D} \\
 &= \bar{B}(\bar{A} + A\bar{D}) + \bar{A}B\bar{C}\bar{D} \quad (*) \\
 &= \bar{B}(\bar{A} + \bar{D}) + \bar{A}B\bar{C}\bar{D} = \\
 &= \bar{A}\bar{B} + \bar{B}\bar{D} + \bar{A}B\bar{C}\bar{D} \\
 &= \bar{A}\bar{B} + \bar{D}(\bar{B} + \bar{A}B\bar{C}) \\
 &= \bar{A}\bar{B} + \bar{D}(\bar{B} + B\bar{A}\bar{C}) \quad (*) \\
 &= \bar{A}\bar{B} + \bar{D}\bar{B} + \bar{A}\bar{C}\bar{D} \\
 &>> F = \bar{A}\bar{B} + \bar{B}\bar{D} + \bar{A}\bar{C}\bar{D}
 \end{aligned}$$


>> SUM OF PRODUCT FORM

NOTE:  $A + \bar{A}B = A + B$  (Rule 11)

## 5. LOGIC DIAGRAM

ASSUMING  $\bar{A}, \bar{B}, \bar{C}, \bar{D}$  ARE AVAILABLE AS INPUTS, WE CAN IMPLEMENT THIS 3 WAYS:

### (a) AND-OR CONFIGURATION

 

### (b) NAND CONFIGURATION:


$$F = \bar{A}\bar{B} + \bar{B}\bar{D} + \bar{A}\bar{C}\bar{D}$$

$$\bar{F} = \overline{\bar{A}\bar{B} + \bar{B}\bar{D} + \bar{A}\bar{C}\bar{D}}$$

$$= \overline{\bar{A}\bar{B}} \cdot \overline{\bar{B}\bar{D}} \cdot \overline{\bar{A}\bar{C}\bar{D}} \quad (\text{De Morgan})$$

$$F = \overline{\bar{F}}$$
 
$$= \overline{\overline{\bar{A}\bar{B}} \cdot \overline{\bar{B}\bar{D}} \cdot \overline{\bar{A}\bar{C}\bar{D}}}$$




**(c) NOR CONFIGURATION:**

$$F = \bar{A}\bar{B} + \bar{B}\bar{D} + \bar{A}\bar{C}\bar{D}$$

$$= \overline{A+B} + \overline{B+D} + \overline{A+C+D} \quad (\text{DM})$$
 
$$\overline{\overline{F}} = F = \overline{\overline{\overline{A+B} + \overline{B+D} + \overline{A+C+D}}}$$



**NOTE:** MORE GATES >>> **LONGER** PROPAGATION DELAYS, i.e. TIME FOR SIGNAL TO GO FROM INPUT TO OUTPUT

## **MINIMISATION USING KARNAUGH MAPS**

**WE HAVE SEEN THAT MINIMISATION USING BOOLEAN ALGEBRA IS A BIT CUMBERSOME.**

**WE CAN REPRESENT ANY LOGICAL EXPRESION ON A DIAGRAM CALLED A KARNAUGH MAP.**

**THIS MAP PROVIDES A SYSTEMATIC METHOD OF SIMPLYFYING A BOOLEAN FUNCTION TO PRODUCE THE SIMPLEST SUM OF PRODUCTS EXPRESION**

### **KARNAUGH MAP FORMAT:**

**FOR N VARIABLES WE HAVE  $2^N$  COMBINATIONS, EACH COMBINATION IS CONTAINED IN A KARNAUGH CELL**

**FOR 2 VARIABLES A, B:**

$2^2 = 4$  PRODUCTS >> 4 CELLS:

$\bar{A}\bar{B}$ ,  $\bar{A}B$ ,  $A\bar{B}$  AND  $AB$ . THIS IS REPRESENTED IN A KARNAUGH MAP AS FOLLOWS:

	$\bar{B}$	$B$
$\bar{A}$	$\bar{A}\bar{B}$	$\bar{A}B$
$A$	$A\bar{B}$	$AB$

THE KARNAUGH MAP IS FILLED IN BY PUTTING A “1” IN EACH CELL THAT LEADS TO A “1” OUTPUT. “0” IS PLACED IN ALL THE OTHER CELLS.

**EXAMPLE:**

(a) REPRESENT  $F = \bar{X}\bar{Y}$  BY ITS KARNAUGH MAP

	$\bar{X}$	$X$
$\bar{Y}$	1	0
$Y$	0	0

$F = 1$  WHEN  $\bar{X}\bar{Y}$  OCCURS

OTHER >>  $F = 0$



(a) REPRESENT  $F = \bar{X}Y + X\bar{Y}$

	$\bar{X}$	X
$\bar{Y}$	0	1
Y	1	0

**F=1** FOR PRODUCT TERMS  $\bar{X}Y$ ,  $X\bar{Y}$  ONLY.

THE EXPRESSION FOR “F” MUST BE WRITTEN “**SUM-OF-PRODUCTS**” FORM TO BEGIN WITH.

**FOR 3 VARIABLES A,B,C**

$2^3 = 8$  PRODUCT TERMS >> **8 CELLS**

	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
$\bar{A}$	$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}C$	$\bar{A}BC$	$\bar{A}B\bar{C}$
A	$A\bar{B}\bar{C}$	$A\bar{B}C$	ABC	$AB\bar{C}$

**EXAMPLE:**


$$F = \bar{A}\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C$$

DO AS EXERCISE.

**RESULT:**

	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
$\bar{A}$	0	1	0	0
A	1	1	0	0

 **NOTE: WHEN MOVING HORIZONTALLY OR VERTICALLY WE SHOULD ONLY ENCOUNTER A CHANGE IN 1 VARIABLE.**



## FOR 4 VARIABLES A,B,C,D

$2^4 = 16$  PRODUCT TERMS  $\gg$  16 CELLS

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	$\bar{A}\bar{B}\bar{C}\bar{D}$	$\bar{A}\bar{B}\bar{C}D$	$\bar{A}\bar{B}C\bar{D}$	$\bar{A}\bar{B}CD$
$\bar{A}B$	$\bar{A}B\bar{C}\bar{D}$	$\bar{A}B\bar{C}D$	$\bar{A}BC\bar{D}$	$\bar{A}BCD$
$AB$	$AB\bar{C}\bar{D}$	$AB\bar{C}D$	$ABC\bar{D}$	$ABCD$
$A\bar{B}$	$A\bar{B}\bar{C}\bar{D}$	$A\bar{B}\bar{C}D$	$A\bar{B}C\bar{D}$	$A\bar{B}CD$

### EXAMPLE:

A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

$$F = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}CD \\ + \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}BC\overline{D}$$

**K-MAP:**

		CD			
		00	01	11	10
AB	00	1	1	0	0
	01	0	1	0	1
	11	0	0	1	0
	10	0	1	0	1

**NOTE:** FOR A 4 VARIABLE K-MAP EACH CELL HAS 4 ADJACENT CELLS

**DON'T FORGET THAT THE K-MAP IS CONSIDERED CONTINUOUS (ROLLED OVER) SO THAT THE TOP ROW IS ADJACENT TO THE BOTTOM ROW AND THE RIGHT COLUMN IS ADJACENT TO THE LEFT COLUMN**

**EXAMPLE:** THE 4 CELLS ADJACENT TO  $\bar{A}\bar{B}\bar{C}\bar{D}$  ARE  $A\bar{B}\bar{C}\bar{D}$ ,  $\bar{A}B\bar{C}\bar{D}$ ,  $\bar{A}\bar{B}C\bar{D}$  AND  $\bar{A}\bar{B}C\bar{D}$

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	●	#		#
$\bar{A}B$	#			
$AB$				
$A\bar{B}$	#			

## MINIMISATION BY GROUPING CELLS

WE CAN MINIMISE ANY BOOLEAN EXPRESSION BY GROUPING ADJACENT CELLS CONTAINING “1”s ACCORDING TO THE FOLLOWING RULES:

1. ADJACENT CELLS ARE CELLS THAT ONLY DIFFER BY A **SINGLE** VARIABLE. >> E.G. **ABCD** AND **ABC $\bar{D}$**
2. THE “1”s IN ADJACENT CELLS MUST BE COMBINED IN GROUPS OF  $2^N$ , I.E. 1,2,4,8,16 ... ETC.
3. EACH **GROUP OF “1”s** SHOULD BE **MAXIMISED** TO INCLUDE THE LARGEST NUMBER OF ADJACENT CELLS POSSIBLE IN ACCORDANCE WITH **RULE 2**
4. EVERY “1” ON THE MAP MUST BE INCLUDED IN **AT LEAST ONE GROUP** (OR **SUBCUBE**). THERE CAN BE OVERLAPPING GROUPS IF THEY INCLUDE NON\_COMMON “1”s

PROCEDURE: WE DRAW A LOOP ABOUT THE CELLS IN ORDER TO DEFINE OUR SUBCUBE.

## EXAMPLES:

		CD			
		00	01	11	10
AB	00	0	0	1	1
	01	1	1	1	1
	11	1	1	1	1
	10	0	1	0	0

		$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
		$\bar{A}$	0	0	0
A	1	1	0	0	

		$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
		$\bar{A}$	0	0	0
A	1	0	0	1	

		$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
		$\bar{A}$	1	0	0
A	1	0	0	1	

## EXERCISE:

**DRAW THE SUBCUBES FOR THE FOLLOWING EXPRESSIONS:**

(a)  $F = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD$

(b)  $F = \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}BC\bar{D} + \bar{A}BCD$   
 $+ AB\bar{C}\bar{D} + AB\bar{C}D + ABC\bar{D} + ABCD$

(a)

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	1	0	0	1
$\bar{A}B$	0	0	0	0
$AB$	0	0	0	0
$A\bar{B}$	1	0	0	1

(b)

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0	0	0	0
$\bar{A}B$	1	1	1	1
$AB$	1	1	1	1
$A\bar{B}$	0	0	0	0



## **SYMPLIFYING THE EXPRESSION**

1. EACH SUBCUBE OF “1”s CREATES A PRODUCT TERM COMPOSED OF ALL VARIABLES THAT APPEAR IN **ONLY ONE FORM** (COMPLEMENTED OR NOT) WITHIN THE GROUP. VARIABLES THAT APPEAR BOTH **UNCOMPLEMENTED** AND **COMPLEMENTED** ARE ELLIMINATED


I.E. >> THE ONE THAT CHANGES WE **DROP**

2. THE **FINAL** SIMPLIFIED EXPRESSION IS FORMED BY **SUMMING** THE PRODUCT TERMS OF ALL THE SUBCUBES

**THIS WILL BECAME CLEARER  
AFTER WE LOOK AT SOME  
EXAMPLES.**

EXAMPLES:

1.

 


$$F = B + \bar{A}C + A\bar{C}D$$

 1. FROM THE 8 CELL GROUP THE PRODUCT TERM IS **B**, WITH THE REFERENCE TO RULE 1, **A** AND  $\bar{A}$ , **C** AND  $\bar{C}$ , **D** AND  $\bar{D}$  ALL APPEAR. >> THEY ARE ELLIMINATED FROM THE PRODUCT TERM; HENCE WE END UP WITH **B**.
2. SIMILARLY IN THE 4 CELL SUBCUBE **D,  $\bar{D}$**  AND **B,  $\bar{B}$**  ARE ELLIMINATED TO LEAVE US WITH  $\bar{A}C$ .
3. IN THE 2 CELL SUBCUBE, **B,  $\bar{B}$**  ARE ELLIMINATED TO LEAVE  $A\bar{C}D$

THIS CAN BE UNDERSTOOD BY REMEMBERING THE FOLLOWING **BOOLEAN RULE**:

$$AX + A\bar{X} = A(X + \bar{X}) = A \cdot 1 = A$$



ELIMINATE

**FOR EXAMPLE:**

$$A\bar{B}\bar{C}D + A\bar{B}C\bar{D} = A\bar{C}D(B + \bar{B}) = A\bar{C}D$$

$$\begin{aligned} &\bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}BCD + \bar{A}B\bar{C}\bar{D} = \\ &= \bar{A}\bar{B}C(D + \bar{D}) + \bar{A}BC(D + \bar{D}) = \\ &= \bar{A}\bar{B}C + \bar{A}BC = \\ &= \bar{A}C(B + \bar{B}) = \bar{A}C \end{aligned}$$

**IN GENERAL, A SUBCUBE OF  $2^M$  CELLS IN AN “N” VARIABLE K-MAP WILL HAVE “M” VARIABLES DIFFERING AND THE SUBCUBE CAN BE REPLACED BY ONE PRODUCT CONSISTING OF “N – M” VARIABLES WHICH REMAIN CONSTANT.**

LAST EXAMPLE:

$$N = 4 \ggg A, B, C, D$$

$$2^M = 4 \ggg M = 2$$

$$\gggg 4 - 2 = 2 \text{ VARIABLE PRODUCT} \\ = \bar{A}C$$

EXAMPLES:

$$(a) F = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD \\ + \bar{A}B\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D}$$

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	1	1	1	1
$\bar{A}B$	1	0	0	0
$AB$	0	0	0	0
$A\bar{B}$	1	0	0	1

$$\square \quad \bar{A}\bar{B} \quad \bigcirc \quad \bar{A}\bar{C}\bar{D} \quad \bigcirc \quad \bar{B}\bar{D}$$

$$F = \bar{A}\bar{B} + \bar{A}\bar{C}\bar{D} + \bar{B}\bar{D} \quad \quad \quad \begin{matrix} 3 \\ \text{SUBCUBES} \end{matrix}$$

(b)

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	1	1	0	0
$\bar{A}B$	0	1	0	0
$AB$	0	0	1	0
$A\bar{B}$	0	0	0	0

$\bar{A}\bar{B}\bar{C}$     
   $\bar{A}\bar{C}D$     
   $ABCD$

$$F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{C}D + ABCD$$

**CONCLUDING NOTE: ALWAYS TRY TO OBTAIN THE REPRESENTATION THAT HAS THE FEWER NUMBER OF CUBES.**

EXAMPLE:

BEST

1	1	0	1
0	1	1	1
0	1	1	0
0	0	0	0

1	1	0	1
0	1	1	1
0	1	1	0
0	0	0	0

1	1	0	1
0	1	1	1
0	1	1	0
0	0	0	0

4 SUBCUBES    4 SUBCUBES    3 SUBCUBES

## FEWER SUBCUBES:

>> FEWER PRODUCT TERMS

>> FEWER GATES

>> MAXIMISE THE SIZE OF SUBCUBES

>> SMALLER PRODUCT TERMS

AT THIS STAGE YOU SHOULD BE ABLE TO MINIMISE A BOOLEAN EXPRESSION BY:

- **BOOLEAN ALGEBRA**
- **KARNAUGH MAP REDUCTION TECHNIQUES**

## **NUMBER SYSTEMS**

**IN ANY NUMBER SYSTEM, THE POSITION OF EACH OF THE DIGITS INDICATES THE MAGNITUDE OF THE QUANTITY REPRESENTED AND CAN BE ASSIGNED A WEIGHT.**

**THE VALUE OF THE NUMBER IS THE SUM OF THE DIGIT TIMES THEIR RESPECTIVE COLUMN WEIGHT.**

### **EXAMPLE – DECIMAL NUMBERS**

$$**23 = 2 * 10 + 3 * 1 = 20 + 3**$$

**I.E. >> DIGIT 2 HAS A WEIGHT OF 10**

**3 HAS A WEIGHT OF 1**

**AS INDICATED BY THEIR RESPECTIVE POSITIONS**

**THE BASE OF A NUMBER SYSTEM IS THE NUMBER OF DIFFERENT DIGITS THAT CAN OCCUR IN EACH POSITION**

## **DECIMAL SYSTEM = BASE 10**

10 DIGITS >>> 0 → 9

E.G.  $26_{10} = 26$

## **HEXADECIMAL SYSTEM = BASE 16**

16 DIGITS >>> 0 → 9, A → F

E.G.  $3A_{16}$

## **BINARY NUMBERS**

THE **BINARY** NUMBER SYSTEM HAS A BASE OF **2**, THE TWO BINARY DIGITS ARE **0** AND **1**

EACH **B**INARY **D**IGIT **I**S CALLED A **BIT**

THE POSITION OF A BIT DETERMINES ITS WEIGHT BUT NOW THE WEIGHT ASCENDS IN POWERS OF 2.

### **EXAMPLES:**

**DECIMAL:**  $11_{10} = 1 * 10^1 + 1 * 10^0$



## **BINARY**

$$\begin{aligned} 101_2 &= 1*2^2 + 0*2^1 + 1*2^0 = \\ &= 4 + 0 + 1 = 5_{10} \end{aligned}$$

$$\begin{aligned} 1010_2 &= 1*2^3 + 0*2^2 + 1*2^1 + 0*2^0 \\ &= 8 + 0 + 2 + 0 = 10_{10} \end{aligned}$$

$$\begin{aligned} 11.011_2 &= 1*2^1 + 1*2^0 + 0*2^{-1} + 1*2^{-2} + 1*2^{-3} \\ &= 2 + 1 + 0 + \frac{1}{2^2} + \frac{1}{2^3} = 3\frac{3}{8} \end{aligned}$$

## **IN GENERAL:**

$$A_n A_{n-1} \dots A_1 A_0 A_{-1} A_{-2} \dots A_{-m}$$

$$\begin{aligned} &= A_n * 2^n + A_{n-1} * 2^{n-1} + \dots + A_1 * 2^1 + A_0 * 2^0 \\ &\quad + A_{-1} * 2^{-1} + A_{-2} * 2^{-2} + \dots + A_{-m} * 2^{-m} \end{aligned}$$

**WE FOLLOW THE ABOVE PROCEDURE  
WHEN WE WISH TO CONVERT FROM  
BINARY TO DECIMAL FORM**

## DECIMAL TO BINARY CONVERSION

TO CONVERT FROM DECIMAL TO BINARY WE REPEATEDLY **DIVIDE BY 2** THE **DECIMAL NUMBER**, AND THE **REMAINDERS** ARE THE **BITS** OF THE RESULTING **BINARY NUMBER**

EXAMPLES:

1.	$19_{10}$	$19 : 2$	•	
		$9 : 2$	1	LSB
		$4 : 2$	1	
		$2 : 2$	0	
		$1 : 2$	0	
		0	1	MSB
			↑	
				REMAINDER


↑  
READ  
UP

$$19_{10} = 10011_2$$

NOTE THE POSITION OF THE DECIMAL POINT, YOU **READ UP** FROM THE **MSB**

**MSB = MOST SIGNIFICANT BIT**

**LSB = LEAST SIGNIFICANT BIT**

2.	$28_{10}$	$28 : 2$	•	
		$14 : 2$	<b>0</b>	LSB
		$7 : 2$	<b>0</b>	
		$3 : 2$	<b>1</b>	
		$1 : 2$	<b>1</b>	
		<b>0</b>	<b>1</b>	

$$28_{10} = 11100_2$$

### DECIMAL FRACTIONS:

THE ABOVE DESCRIBED METHOD DOES NOT WORK FOR FRACTIONS. HERE WE REPEATEDLY **MULTIPLY** THE FRACTION BY **TWO** (UNTIL THE FRACTIONAL PRODUCT IS ZERO) AND THE **WHOLE NUMBER CARRYS** ARE THE BITS OF THE RESULTING BINARY NUMBER.

### EXAMPLE:

$.4375_{10}$	$.4375 * 2$	•	
	$.8750 * 2$	CARRY	<b>0</b> MSB
READ DOWN ↓	$.7500 * 2$	CARRY	<b>1</b>
	$.5000 * 2$	CARRY	<b>1</b>
	$.0000$	CARRY	<b>1</b> LSB

$$.4375_{10} = .0111_2$$

AGAIN, NOTE THE DECIMAL POINT POSITION AND **READ DOWN**.

## MIXED DECIMAL NUMBERS

THESE MUST BE SPLIT INTO THEIR **WHOLE** AND **FRACTIONAL** PARTS, EACH PART **CONVERTED SEPARATELY** AND THE TWO PARTS ARE THEN **ADDED**.

### EXAMPLE

$$13.75_{10} = 13_{10} + .75_{10}$$

13 : 2	•		.75 * 2	•
6 : 2	1	↑	.50 * 2	1
3 : 2	0		.00	1
1 : 2	1			
0	1			

$$13.75_{10} = 1101.11_2$$

# BINARY NUMBERS

BINARY				DECIMAL
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9
1	0	1	0	10
1	0	1	1	11
1	1	0	0	12
1	1	0	1	13
1	1	1	0	14
1	1	1	1	15
$2^3$	$2^2$	$2^1$	$2^0$	
MSB			LSB	

## BINARY ADDITION

SIMILAR TO DECIMAL ADDITION BUT SIMPLER AS ONLY 0's AND 1's ARE ALLOWED. THE FOUR BASIC RULES ARE:

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 10_2 \gg \text{i.e. } 0 \text{ WITH A CARRY OF } 1$$

### EXAMPLES:

	$\begin{array}{r} \text{(a)} \quad 11_2 + \\ \quad \underline{11_2} \\ 110_2 \end{array}$	$\gg$	$\begin{array}{r} 3_{10} + \\ \quad \underline{3_{10}} \\ 6_{10} \end{array}$		$\text{i.e. } 1+1+1 = 1 \\ \text{WITH A} \\ \text{CARRY } 1$
--	---	-------	---	--	--

	$\begin{array}{r} \text{(b)} \quad 1111 + \\ \quad \underline{10100} \\ 100011_2 \end{array}$	$\gg$	$\begin{array}{r} 15 + \\ \quad \underline{20} \\ 35_{10} \end{array}$
--	---	-------	--

	$\begin{array}{r} \text{(c)} \quad 11.01 + \\ \quad \underline{101.11} \\ 1001.00_2 \end{array}$	$\gg$	$\begin{array}{r} 3.25 + \\ \quad \underline{5.75} \\ 9.00_{10} \end{array}$
--	--	-------	--


## LOGIC CIRCUITS

### THE HALF ADDER:

TO ADD 2 LEAST SIGNIFICANT BITS (LSB) WE DO NOT NEED A CARRY INPUT FROM A PREVIOUS STAGE.

>> WE ONLY NEED A **HALF ADDER**

 THIS WILL HAVE TWO INPUTS  $A_0$ ,  $B_0$  AND TWO OUTPUTS  $S_0$  AND  $C_0$



$S_0$  : **SUM OUT**


$C_0$ : **CARRY OUT**

THE **LOGIC EQUATIONS** ARE:

$$S_0 = \bar{A}_0 B_0 + A_0 \bar{B}_0 = A \oplus B > \text{(XOR Gate)}$$

$$C_0 = A_0 B_0 > \text{(AND Gate)}$$

 **THE LOGIC DIAGRAM CAN ALSO BE EXPRESSED AS FOLLOWS:**



### **THE FULL ADDER:**

FOR ALL OTHER BITS (EXCEPT THE LSB) A HALF ADDER WILL NOT SUFFICE BECAUSE THERE MAY BE A CARRY INPUT FROM A PREVIOUS STAGE.




**A FULL ADDER HAS 3 INPUTS:  $A_K$ ,  $B_K$ ,  $C_{K-1}$**

**AND 2 OUTPUTS:  $S_K$ ,  $C_K$**

**$C_{K-1}$  = CARRY IN FROM THE PREVIOUS STAGE**

**$C_K$  = CARRY OUT TO THE NEXT STAGE**

 

$A_k$	$B_k$	$C_{k-1}$	$S_k$	$C_k$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

**THE LOGIC EQUATIONS ARE:**

$$S_K = \bar{A}_K \bar{B}_K C_{K-1} + \bar{A}_K B_K \bar{C}_{K-1} + A_K \bar{B}_K \bar{C}_{K-1} + A_K B_K C_{K-1}$$

$$C_K = \bar{A}_K B_K C_{K-1} + A_K \bar{B}_K C_{K-1} + A_K B_K \bar{C}_{K-1} + A_K B_K C_{K-1}$$

**K-MAP FOR  $S_K$ :**

		<b><math>A_K B_K</math></b>			
		0 0	0 1	1 1	1 0
<b><math>C_{K-1}</math></b>	0	0	1	0	1
	1	1	0	1	0


**NO SIMPLIFICATION POSSIBLE**

### K-MAP FOR $C_K$ :

		$A_K B_K$			
		00	01	11	10
$C_{K-1}$	0	0	0	1	0
	1	0	1	1	1

$$C_K = B_K C_{K-1} + A_K B_K + A_K C_{K-1}$$

 **THE LOGIC DIAGRAM FOR A FULL ADDER IS:**




## FULL ADDER USING HALF ADDERS

ONE HALF ADDER ADDS  $A_K$  TO  $B_K$  TO GIVE AN INTERMEDIATE SUM  $S'_K$  AND CARRY  $C'_K$

ANOTHER HALF ADDER ADDS  $S'_K$  AND  $C_{K-1}$  TO GIVE THE FINAL SUM  $S_K$  AND ANOTHER INTERMEDIATE CARRY  $C''_K$

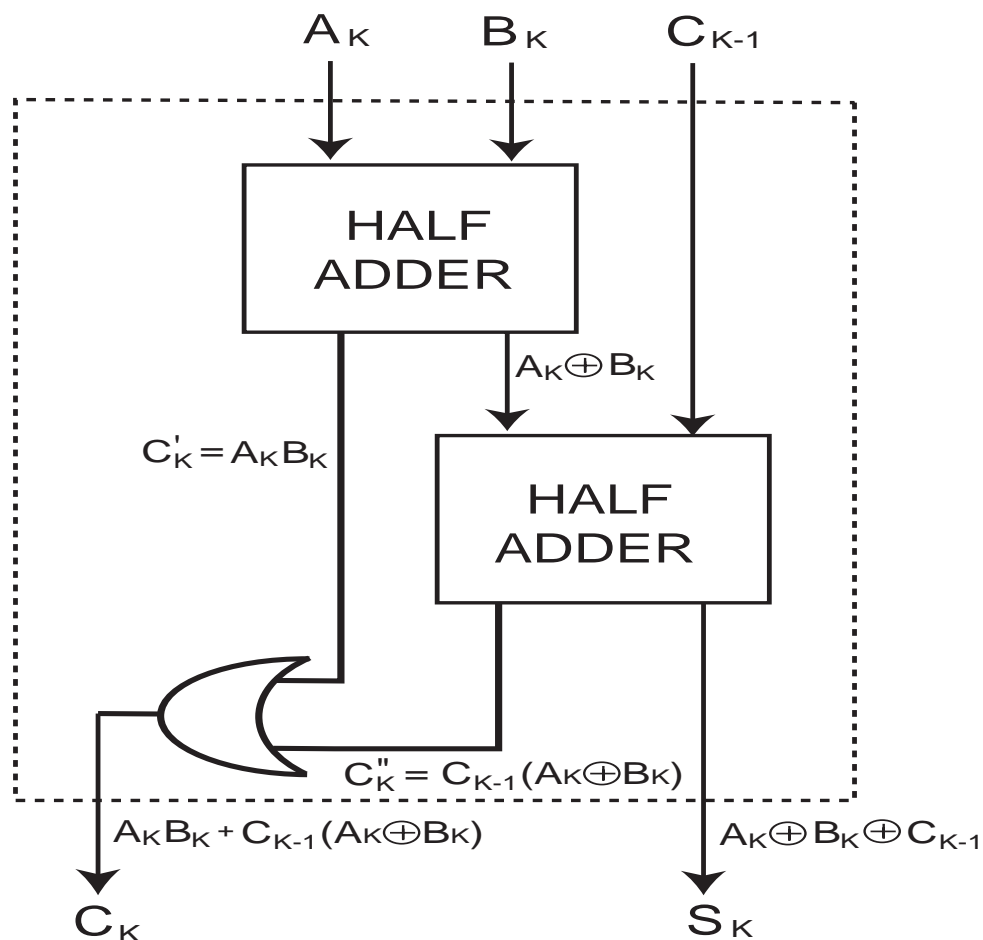THERE WILL BE A FINAL CARRY IF EITHER  $C'_K$  OR  $C''_K$  ARE "1"



REMEMBER THE BOOLEAN OPERATION  
FOR **HALF ADDER**:

$$S'_K = A_K \oplus B_K$$

$$C'_K = A_K B_K$$

FOR FULL ADDER:

$$S_K = A_K \oplus B_K \oplus C_{K-1}$$

$$C_K = A_K B_K + C_{K-1}(A_K \oplus B_K)$$

PROOF:

$$S_K = \bar{A}_K \bar{B}_K C_{K-1} + \bar{A}_K B_K \bar{C}_{K-1} + A_K \bar{B}_K \bar{C}_{K-1}$$

$$+ A_K B_K C_{K-1} = C_{K-1}(\bar{A}_K \bar{B}_K + A_K B_K) +$$

$$+ \bar{C}_{K-1}(\bar{A}_K B_K + A_K \bar{B}_K) = C_{K-1}(\overline{\bar{A}_K \oplus \bar{B}_K}) +$$

$$+ \bar{C}_{K-1}(A_K \oplus B_K) = A_K \oplus B_K \oplus C_{K-1}$$

$$C_K = \bar{A}_K B_K C_{K-1} + A_K \bar{B}_K C_{K-1} + A_K B_K \bar{C}_{K-1}$$

$$+ A_K B_K C_{K-1} =$$

$$= A_K B_K (C_{K-1} + \bar{C}_{K-1}) + C_{K-1}(\bar{A}_K B_K + A_K \bar{B}_K) =$$

$$= A_K B_K + C_{K-1}(A_K \oplus B_K)$$


## THE PARALLEL ADDER:

ALSO CALLED **RIPPLE CARRY** ADDER  
USED TO ADD **TWO N-BIT** NUMBERS.

IT CONSISTS OF **N FULL ADDERS**  
WHERE THE CARRY OUTPUT OF EACH  
STAGE IS THE CARRY IN OF THE NEXT  
STAGE.

### **EXAMPLE: 4-BIT PARALLEL ADDER**

ADD  $A_3A_2A_1A_0$  AND  $B_3B_2B_1B_0$

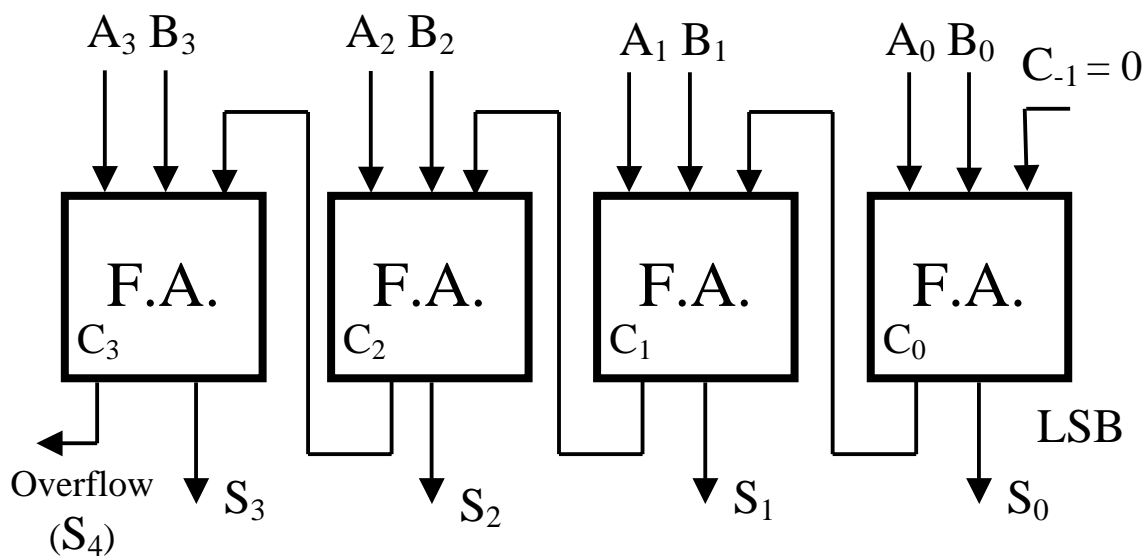

$C_3 = 1 \gg \gg$  OVERFLOW

E.G.  $A = \mathbf{1010}$  ( $10_{10}$ )

$B = \mathbf{1001}$  ( $9_{10}$ )

Overflow  $\leftarrow (\mathbf{1})0011 \rightarrow 3_{10}$

## **BINARY NEGATIVE NUMBERS**

IN THE DECIMAL NUMBER SYSTEM **NEGATIVE** NUMBERS ARE DENOTED BY A **MINUS** SIGN. SINCE **ONLY “0”s AND “1”s ARE ALLOWED BY BOOLEAN ALGEBRA** WE MUST USE THESE DIGITS TO REPRESENT POSITIVE AND NEGATIVE NUMBERS.

THERE ARE 3 DIFFERENT FORMS TO REPRESENT POSITIVE AND NEGATIVE NUMBERS IN BINARY

### **1. SIGNED MAGNITUDE FORM:**

- THE MAGNITUDE OF THE NUMBER IS IN NORMAL BINARY FORM
- THE EXTRA LEADING BIT IS USED FOR THE SIGN:
  - “0” >>> POSITIVE
  - “1” >>> NEGATIVE
- THIS REPRESENTATION IS ALSO CALLED **SIGN PLUS MAGNITUDE**





## IF WE HAVE A 5-BIT 1's COMPLEMENT NUMBER THEN:

- FIRST BIT (MSB) >>> SIGN
- 4 OTHER BITS >>> MAGNITUDE

0	1111	+15 <sub>10</sub>	
0	1110	+14 <sub>10</sub>	
0	1101	+13 <sub>10</sub>	
	⋮		
0	0001	+1 <sub>10</sub>	
<b>0</b>	<b>0000</b>	→	ZERO
<b>1</b>	<b>1111</b>	→	AMBIGUITY
1	1110	-1 <sub>10</sub>	
1	1101	-2 <sub>10</sub>	
	⋮		
1	0001	-14 <sub>10</sub>	
1	0000	-15 <sub>10</sub>	

## ONE'S COMPLEMENT ADDITION

### (a) ADDITION OF 2 POSITIVE NUMBERS


**E.G.**

+7	00111	+11	01011
<u>+5</u>	<u>00101</u>	<u>+4</u>	<u>00100</u>
+12	01100	+15	01111

### (b) ADDITION OF POSITIVE AND NEGATIVE NUMBERS

**E.G.**


+3	0 0011
<u>-12</u>	<u>1 0011</u>
-9	1 0110


NEGATIVE  
NUMBER

$$= 3 + (-12)$$


$$1\ 0110 \gggg - \overline{[0110]} = -1001 = -9$$

+9	0 1001
<u>-4</u>	<u>1 1011</u>
+5	(1)0 0100

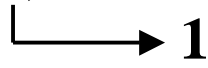
ADD END  
AROUND  
CARRY

+5 = 0 0101



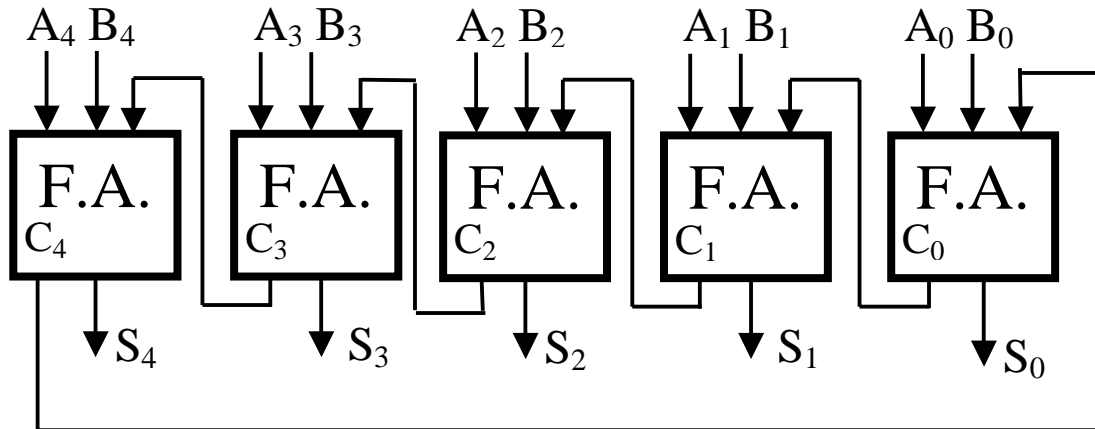

END AROUND CARRY

**RANGE: +15 ÷ -15**

THE **MOST** SIGNIFICANT CARRY OUTPUT IS **ALWAYS** CONNECTED TO THE **LEAST** SIGNIFICANT CARRY INPUT

THERE IS AN END AROUND CARRY **IF**  $C_4=1$ , OTHERWISE THE **LEAST** SIGNIFICANT CARRY INPUT IS **0**.

### 3. TWO'S COMPLEMENT FORM:

MOST POPULAR BINARY FORM

SIMILAR TO 1's COMPLEMENT BUT FOR NEGATIVE NUMBERS ADD "1" TO THE 1's COMPLEMENT RESULT

$$\begin{array}{rcl} \text{E.G.} & +5 & = 0\ 0101 \\ & -5 & = 1\ 1010 \quad \text{1's COMPLEMENT} \\ & & \underline{\qquad\qquad\qquad 1} \\ & -5 & = 1\ 1011 \quad \text{2's COMPLEMENT} \end{array}$$

$$\begin{array}{rcl} & +0 & = 0\ 0000 \\ & & \quad 1\ 1111 \quad \text{INVERT} \\ & & \quad \underline{\qquad\qquad\qquad 1} \quad \text{ADD 1} \\ & (1) & 0\ 0000 = -0 \end{array}$$

**\*\*\* UNAMBIGUOUS ZERO !**

+16 >>> NOT POSSIBLE

-16 >>> 1 0000

**(a) ADDING TWO POSITIVE NUMBERS**

STRAIGHTFORWARD PROVIDING THERE IS NO OVERFLOW

**E.G. 5-BIT NUMBERS**

+5	0 0101	+12	0 1100
<u>+9</u>	<u>0 1001</u>	<u>+3</u>	<u>0 0011</u>
+14	0 1110	+15	0 1111

**(b) ADDING TWO NEGATIVE NUMBERS**

-6	1 1010	-12	1 0100
<u>-9</u>	<u>1 0111</u>	<u>-4</u>	<u>1 1100</u>
-15	(1) 1 0001	-16	(1) 1 0000

↓  
**IGNORE**
↓  
**IGNORE**

**(c) ADDING POSITIVE AND NEGATIVE NUMBERS**

-9	1 0111	+12	0 1100
<u>+3</u>	<u>0 0011</u>	<u>-4</u>	<u>1 1100</u>
-6	1 1010	+8	(1) 0 1000

+15	0 1111	-8	1 1000
<u>-1</u>	<u>1 1111</u>	<u>+8</u>	<u>0 1000</u>
+14	(1) 0 1110	0	(1) 0 0000

**ALWAYS IGNORE THE MOST SIGNIFICANT CARRY**

- **ADVANTAGE OVER 1's COMPLEMENT IN THAT NO END AROUND CARRY NEEDED**

**N BITS  $\gg$   $2^N$  NUMBERS MAY BE REPRESENTED (INCLUDING ZERO)**

**4 BITS  $\gg$  16 NUMBERS**

**RANGE:  $-8 \div +7$**

## **OVERFLOW AND UNDERFLOW**

**REMEMBER THE NUMBER OF DIGITS IS RESTRICTED**

**WHEN ADDING NUMBERS OF OPOSITE SIGN THE RESULT CAN NEVER EXCEED THE PERMITTED RANGE**

**BUT WHEN TWO POSITIVE NUMBERS ARE ADDED THE RESULT MAY BE TOO LARGE i.e. OVERFLOW OCCURS**

**E.G.**

0 1101	+13	
<u>0 0101</u>	<u>+5</u>	
1 0010	-14	<<< <b>WRONG</b>

└─→ **OVERFLOW**

<b>A</b>	0 1000	+8	
<b>B</b>	<u>0 1000</u>	<u>+8</u>	
<b>S</b>	1 0000	-16	<<< <b>WRONG</b>

└─→ **OVERFLOW**

IF EACH NUMBER HAS  $N+1$  BITS

$$\text{OVERFLOW} = \bar{A}_N \bar{B}_N S_N$$

**OVERFLOW** INDICATES WE ARE OUTSIDE THE RANGE AND WE CANNOT REPRESENT THE RESULT IN OUR RESTRICTED NUMBER OF BITS



## UNDERFLOW

UNDERFLOW MAY OCCUR WHEN TWO **NEGATIVE** NUMBERS ARE ADDED THE RESULT IS **OUTSIDE THE RANGE**

E.G.

1 0011	-13	
<u>1 1000</u>	<u>-8</u>	
(1) 0 1011	+11	<<< <b>WRONG</b>

A	1 0000	-16	
<u>B</u>	<u>1 1111</u>	<u>-1</u>	
S	(1) 0 1111	+15	<<< <b>WRONG</b>



SHOULD BE **-17** BUT THIS IS **OUTSIDE**  
THE PERMITTED RANGE

IF EACH NUMBER HAS **N+1** BITS

$$\text{UNDERFLOW} = A_N B_N \bar{S}_N$$

## SUBTRACTION

**DIRECT SUBTRACTION** (i.e. NOT USING SPECIAL REPRESENTATIONS TO GENERATE NEGATIVE NUMBERS) CAN BE PERFORMED BY DETERMINING THE **TRUTH TABLE** AND THEN DESIGNING A **LOGIC DIAGRAM**

**THE FOUR BASIC RULES ARE:**


$$0 - 0 = 0$$

$$1 - 1 = 0$$

$$1 - 0 = 1$$

$$0 - 1 = 10_2 - 1 = 1 \text{ WITH A BORROW OF } 1$$

A	B	A - B	BORROW $B_0$
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

 

**HALF SUBTRACTOR**

$$\text{DIFFERENCE} = A - B = A \oplus B$$

$$\text{BORROW} = B_0 = \bar{A}B$$

**FULL SUBTRACTOR:**

A	B	BORROW IN $B_{IN}$	DIFF $A-(B+B_{IN})$	BORROW OUT $B_{OUT}$
0	0	0	<b>0</b>	<b>0</b>
0	0	1	<b>1</b>	<b>1</b>
0	1	0	<b>1</b>	<b>1</b>
0	1	1	<b>0</b>	<b>1</b>
1	0	0	<b>1</b>	<b>0</b>
1	0	1	<b>0</b>	<b>0</b>
1	1	0	<b>0</b>	<b>0</b>
1	1	1	<b>1</b>	<b>1</b>

USING K-MAPS IT CAN BE SHOWN THAT:

$$B_{OUT} = \bar{A}B_{IN} + \bar{A}B + BB_{IN}$$


$$DIFF = \bar{A}\bar{B}B_{IN} + \bar{A}B\bar{B}_{IN} + AB\bar{B}_{IN} + A\bar{B}\bar{B}_{IN}$$

**NOTE:** SUBTRACTION MAY BE DONE MORE ECONOMICALLY BY REPRESENTING THE NEGATIVE NUMBERS USING **2's COMPLEMENT FORM**

**E.G.**  $9 - 6 = 9 + (-6)$
 
## TWO's COMPLEMENT ADDER/SUBTRACTOR

IT IS POSSIBLE TO BUILD A CIRCUIT WHICH ADDS AND SUBTRACTS USING ONLY FULL ADDERS AND SOME ADDITIONAL CIRCUITRY TO GENERATE THE 2's COMPLEMENT WHEN WISH TO DO SUBTRACTION



$\overline{\text{ADD/SUB}} = 0 \gg \text{ADDER}$   
 $= 1 \gg \text{SUBTRACTOR}$

- **XOR GATES ACT AS "TRUE/COMPLEMENT" GATES**
- **INVERT B WHEN  $\overline{\text{ADD/SUB}} = 1$**
- **"1" IS ADDED TO THE LSB TO GENERATE THE 2's COMPLEMENT OF B**