





Principles Of Digital Design

Chapter 4

Simplification of Boolean Functions

- *Karnaugh Maps*
- *Don't Care Conditions*
- *Technology Mapping*
- *Optimization, Conversions, Decomposing, Retiming*

Boolean Cubes for $n = 1, 2, 3,$ and 4

    

Boolean Functions and Boolean Cubes

- Each Boolean n -cube represents a Boolean function of n variables
- Each vertex represents a minterm
- Each m -subcube represents 2^m minterms, $m < n$, with the same $n - m$ literals
- Each m -subcube of 1-minterm represent a product of $n - m$ literals



$$\begin{aligned} &= l_1 l_2 \dots l_{n-m} (x'_{n-m+1} x'_{n-m+2} \dots x'_n + x'_{n-m+1} x'_{n-m+2} \dots x_n + \dots + x_{n-m+1} x_{n-m+2} \dots x_n) \\ &= l_1 l_2 \dots l_{n-m} \end{aligned}$$

- For any Boolean function a prime implicant is a subcube not contained in any other prime implicant
- An essential prime implicant is a subcube that contains a 1-minterm that is not included in any other prime implicant

Representation of Carry and Sum Functions with Boolean Cubes

c_i	x_i	y_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


Truth Table

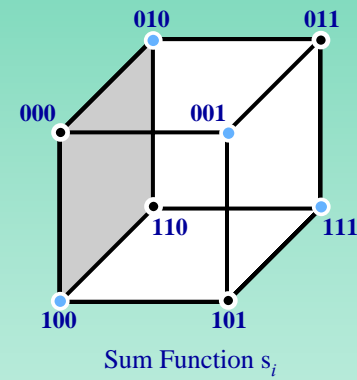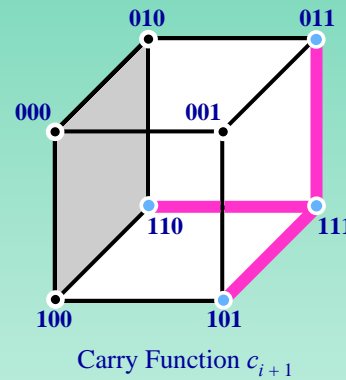


Map Representation

- (Karnaugh) maps define Boolean functions
- Map representation is equivalent to truth tables, Boolean expressions and Boolean cube representation
- Map aid in visually identifying prime implicants and essential prime implicants in each Boolean function
- Maps are used for manual optimization of Boolean functions

 
Boolean Subcubes and Corresponding Karnaugh Maps for $n = 1, 2, 3,$ and 4




$n = 1$

 

$n = 2$

 


$n = 3$

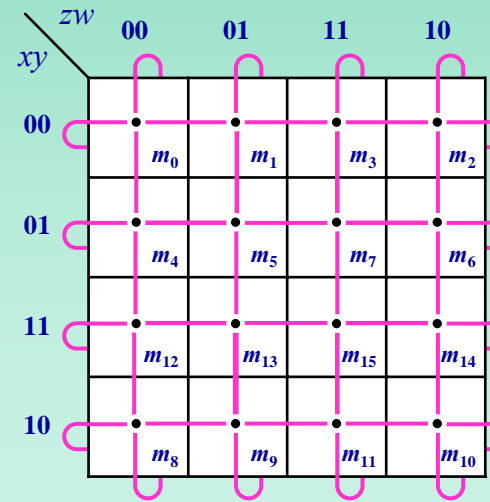


$n = 4$

2-variable Map

 

Map Organization

 


Example of 1-subcubes


Example:

<i>x</i>	<i>y</i>	<i>AND</i>	<i>OR</i>	<i>XOR</i>
0	0	0	0	0
0	1	0	1	1
1	0	0	1	1
1	1	1	1	0


Truth Table

 

AND

 

OR

 


XOR


Three-variable Map

	yz			
	00	01	11	10
x				
0	⁰ $x'y'z'$	¹ $x'y'z$	³ $x'yz$	² $x'yz'$
1	⁴ $xy'z'$	⁵ $xy'z$	⁷ xyz	⁶ xyz'

Map Organization

 

Example of 2-subcubes

 

Example of 1-subcubes

Map Representation of Carry and Sum Functions

c_i	x_i	y_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Truth Table

$c_i \backslash x_i y_i$	00	01	11	10
0	0	0	1	0
1	0	1	1	1

Carry Function c_{i+1}


$c_i \backslash x_i y_i$	00	01	11	10
0	0	1	0	1
1	1	0	1	0

Sum Function s_i


Four-variable Map

		zw			
		00	01	11	10
xy	00	⁰ $x'y'z'w'$	¹ $x'y'z'w$	³ $x'y'zw$	² $x'y'zw'$
	01	⁴ $x'yz'w'$	⁵ $x'yz'w$	⁷ $x'yzw$	⁶ $x'yzw'$
	11	¹² $xyz'w'$	¹³ $xyz'w$	¹⁵ $xyzw$	¹⁴ $xyzw'$
	10	⁸ $xy'z'w'$	⁹ $xy'z'w$	¹¹ $xy'zw$	¹⁰ $xy'zw'$

Map Organization

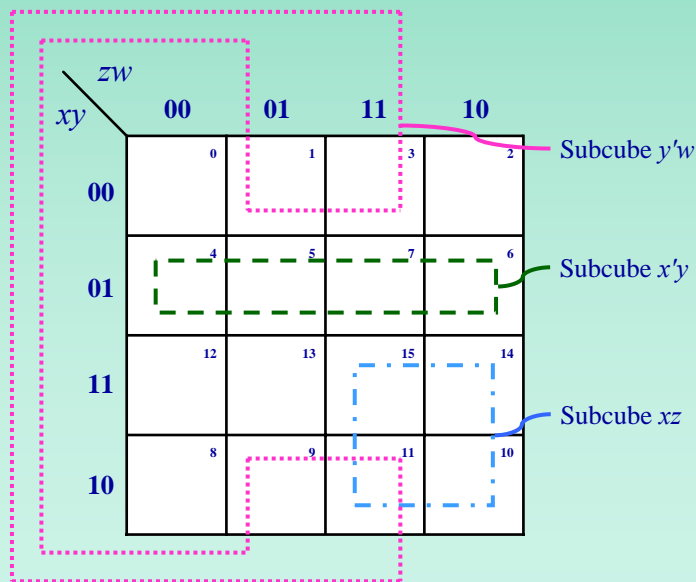

Example of 2-subcubes

 


Example of 3-subcubes

Representation of Greater-than and Less-than Functions in Maps


x_1	x_0	y_1	y_0	Greater Than	Equal	Less Than
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

Truth Table

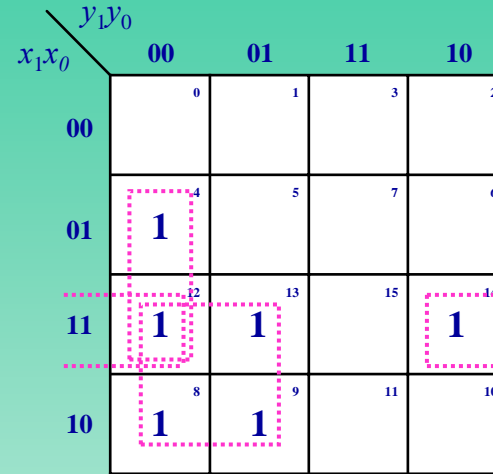

Greater-than Function
 
$$G = x_1y_1' + x_0y_1'y_0' + x_1x_0y_0'$$




Less-than Function

$$L = x_1'y_1 + x_1'x_0'y_0 + x_0'y_1y_0$$

Five-variable Map


xy	v = 0				v = 1			
	zw 00	01	11	10	00	01	11	10
00	0 $x'y'z'w'v'$	1 $x'y'z'wv'$	3 $x'y'zvw'$	2 $x'y'zw'v'$	16 $x'y'z'w'v$	17 $x'y'z'wv$	19 $x'y'zvw$	18 $x'y'zw'v$
01	4 $x'yz'w'v'$	5 $x'yz'wv'$	7 $x'yzvw'$	6 $x'yzw'v'$	20 $x'yz'w'v$	21 $x'yz'wv$	23 $x'yzvw$	22 $x'yzw'v$
11	12 $xyz'w'v'$	13 $xyz'wv'$	15 $xyzvw'$	14 $xyzw'v'$	28 $xyz'w'v$	29 $xyz'wv$	31 $xyzvw$	30 $xyzw'v$
10	8 $xy'z'w'v'$	9 $xy'z'wv'$	11 $xy'zvw'$	10 $xy'zw'v'$	24 $xy'z'w'v$	25 $xy'z'wv$	27 $xy'zvw$	26 $xy'zw'v$

Map Organization

 


Example of 3-subcubes and 4-subcubes

Six-variable Map

 


Map Organization

 

Example of 4-subcubes

Boolean Simplification with Map Method

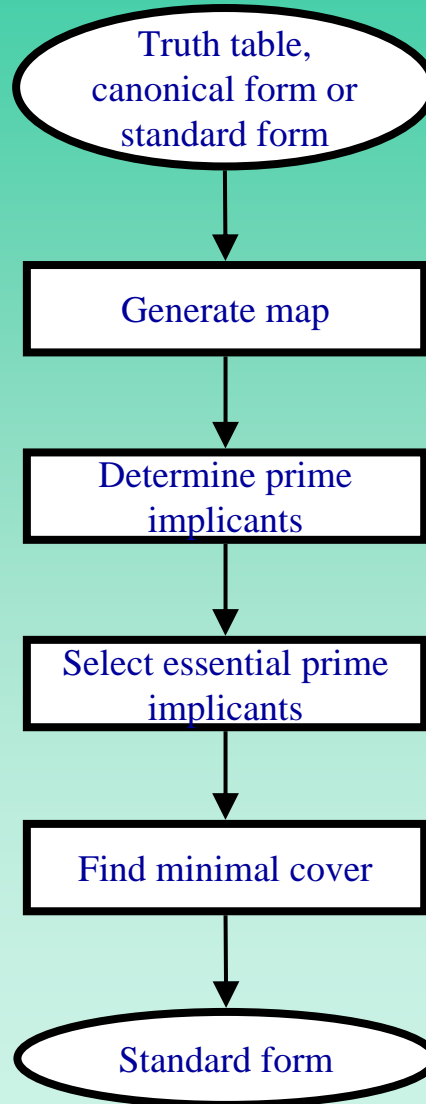

Boolean Simplification with Map Method

Example: Maps method

Problem: Using the map method, simplify the Boolean function

$$F = w'y'z' + wz + xyz + w'y$$

	zw			
	00	01	11	10
xy	00	01	11	10
00	1		1	1
01	1		1	1
11		1	1	
10		1	1	

Map Organization

	zw			
	00	01	11	10
xy	00	01	11	10
00	1		1	1
01	1		1	1
11		1	1	
10		1	1	

Prime Implicants in the Map

PI List: $w'z'$, wz , yz , $w'y$

EPI List: $w'z'$, wz

Cover List: (1) $w'z'$, wz , yz
 (2) $w'z'$, wz , $w'y$

Selection of Prime Implicants

Example: Selection of prime implicants

Problem: Simplify the Boolean function

$$F = w'x'yz' + w'xy + wxz + wx'y' + w'x'y'z'$$

zw \ xy	00	01	11	10
00	0 1	1	3	2 1
01	4	5	7 1	6 1
11	12	13 1	15 1	14
10	8 1	9 1	11	10

PI List: $w'x'z'$, $w'xy$, wxz , $wx'y'$, $x'y'z'$, $wy'z$, xyz , $w'yz'$

EPI List: empty

Cover List: (1) $w'x'z'$, $w'xy$, wxz , $wx'y'$

(2) $x'y'z'$, $wy'z$, xyz , $w'yz'$

Don't-Care Conditions

- **Completely specified functions have a value assigned for every minterm**
- **Incompletely specified functions do not have values assigned for some minterms which are called don't-care minterms (d-minterms) or don't-care conditions**
- **Don't-care minterms can be assigned any value during simplifications in order to simplify Boolean expressions**


Don't-Care Conditions

Example: Don't-care conditions

Problem: Derive Boolean expressions for the 9's complement of a BCD digit

Digits				Nine's Complements					
Decimal	BCD				Decimal	BCD			
	x_3	x_2	x_1	x_0		x_3	x_2	x_1	x_0
0	0	0	0	0	9	1	0	0	1
1	0	0	0	1	8	1	0	0	0
2	0	0	1	0	7	0	1	1	1
3	0	0	1	1	6	0	1	1	0
4	0	1	0	0	5	0	1	0	1
5	0	1	0	1	4	0	1	0	0
6	0	1	1	0	3	0	0	1	1
7	0	1	1	1	2	0	0	1	0
8	1	0	0	0	1	0	0	0	1
9	1	0	0	1	0	0	0	0	0

Nine's-Complement Table

 


Map Representation


Technology Mapping for Gate Arrays

- Gate arrays contain only one type of m -input gate (such as 3-input NOR, 3-input NAND)
- Technology mapping is a transformation of Boolean expressions into a logic schematic containing only this type of gate
- Technology mapping consist of three tasks
 - ◆ Conversion replaces each operator with an operator representing the gate function given in the gate array
 - ◆ Optimization eliminates unnecessary inverters
 - ◆ Decomposition replaces a n -input gate with an m -input gate available in the gate array

Conversion and Optimization

 

Conversion Rules






 


Optimization Rules

• Conversion Procedure:

- ◆ Replace AND and OR gates with NAND or NOR gates by using Rules 1 – 4, and eliminate double inverters whenever possible

Translation of Standard Terms to NAND and NOR Schematics

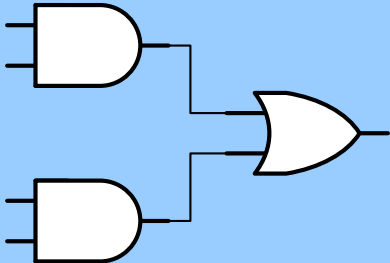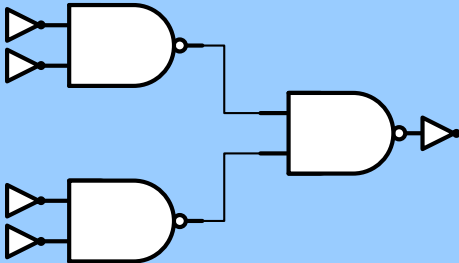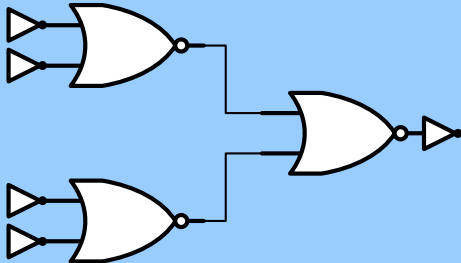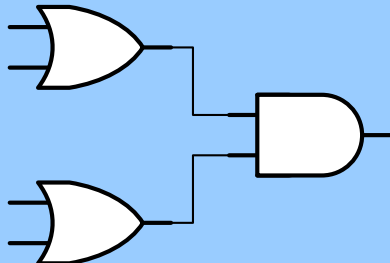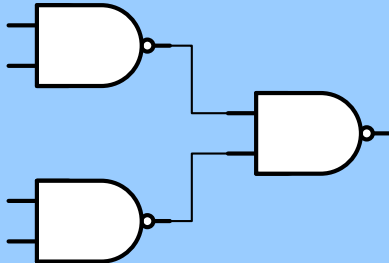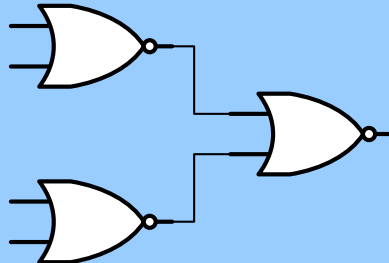Form Type	Standard Form Implementation	NAND Implementation	NOR Implementation
Sum of products			
Product of sums			

Conversion to NAND (NOR) Gates

Example: Conversion to NAND (NOR) gates

Problem: Derive the NAND and NOR implementations of the carry function


$x_i y_i$	00	01	11	10
c_i				
0	0	1	3	2
1	4	5	7	6

Map Definition Carry Function c_{i+1}


$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = (x_i + y_i)(x_i + c_i)(y_i + c_i)$$

Standard Forms

 

NAND Implementation

 


NOR Implementation


Decomposition of 10-input AND Gate into 3-input AND Gates

Level Number	Number of Inputs	Number of Gates
1	10	$\lceil 10 / 3 \rceil = 3$
2	$3 + (10 - 3(\lceil 10 / 3 \rceil)) = 4$	$\lceil 4 / 3 \rceil = 1$
3	$1 + (4 - 3(\lceil 4 / 3 \rceil)) = 2$	$\lceil 2 / 3 \rceil = 1$

Input and Gate Computation on Each Level

 

One Possible Decomposition

 

Alternative Decomposition


Technology Mapping for Gate Arrays

Example: Technology mapping for gate arrays


Problem: Implement the sum function using 3-input NAND gates

$x_i y_i$	00	01	11	10
0	0	1	3	2
1	4	5	7	6


Map Definition Sum Function s_i

 


AND-OR Implementation

 

Conversion to NAND Network

 

OR Gate Decomposition

 

Optimized NAND Network


Design Retiming

Example: Design retiming


Problem: Implement 4-bit carry-look-ahead function

$$c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$$


using 3-input NAND gates

 


AND-OR Implementation

 


Decomposition of AND-OR Implementation

 

Performance Optimized Decomposition

 


 NAND Implementation of Above
Delay = 8.2ns



Performance Optimized NAND Implementation
Delay = 6.4ns

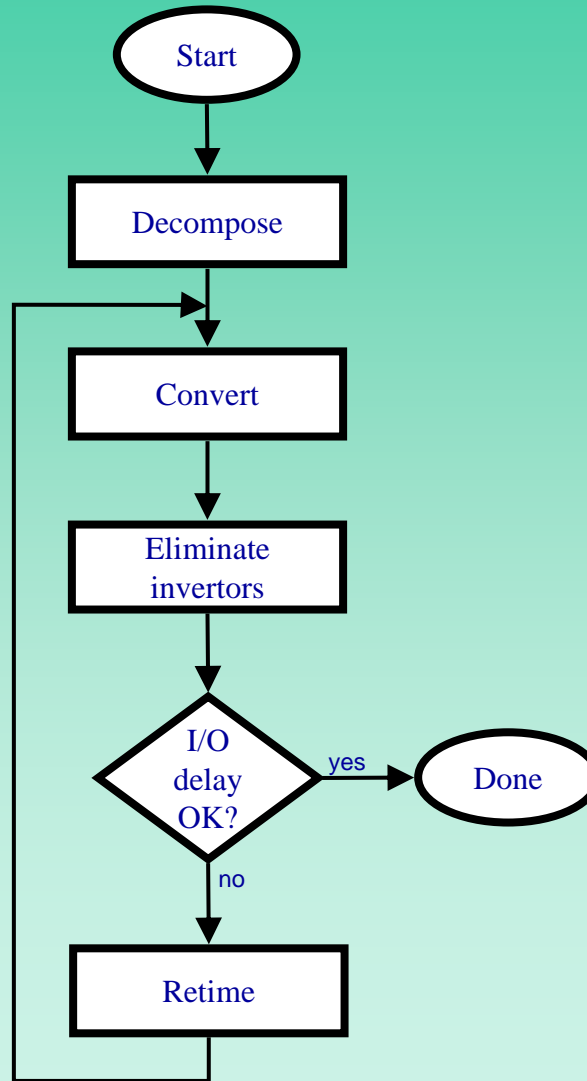Technology Mapping Procedure for Gate Arrays




Technology Mapping for Custom Libraries

- Libraries contain gates with different functions and different delays
- Technology mapping means covering schematic with library gates
- Minimize delay on critical paths
- Minimize cost on non-critical paths


Technology Mapping for Custom Libraries

Example: Technology mapping for custom libraries

 
Problem: Convert the expression $w'z' + z(w + y)$ into a logic schematic using any of the gates defined in the digital logic gates, multiple-input gates, and complex gates libraries



 
AND-OR Implementation (Delay = 7.2ns, Cost = 28)




Alternative A (Delay = 5.4ns, Cost = 20)

 

 
NAND Implementation (Delay = 5.2ns, Cost = 22)



Alternative B (Delay = 3.8ns, Cost = 20)

 


Two Possible Conversions

 

Cost Optimized Alternative B (Delay = 3.8ns, Cost = 18)

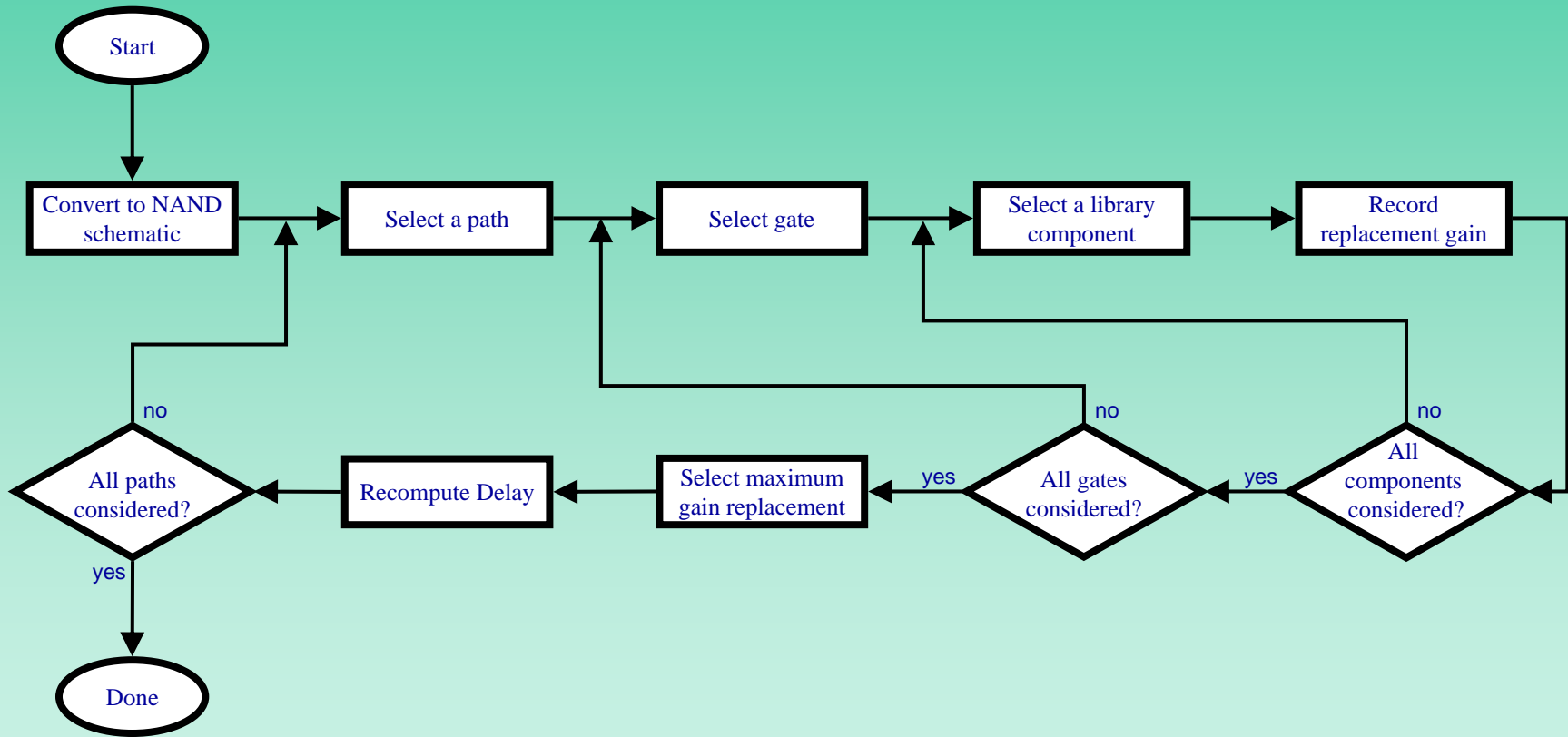Conversion Procedure for Custom Libraries



Chapter Summary

- **Simplification of Boolean functions by**
 - ◆ **Map method (visual)**
- **Technology mapping for gate arrays**
 - ◆ **Decomposition**
 - ◆ **Conversion**
 - ◆ **Optimization**
 - ◆ **Retiming**
- **Technology mapping for custom libraries by schematic covering with complex gates with**
 - ◆ **Time optimization on circuit paths**
 - ◆ **Cost optimization on non-critical paths**